

U 496 BS	Aeç	LIN-IC	3Hz Frequ.-Teiler/Prescaler, 1.4069, 1.CATV Tuner	8-DIP	
U 501 D	Hfo	ROM-IC	2048 Bit	24-DIP	I 1302
U 505 D	Hfo	ROM-IC	8192 Bit, mask-program.	24-DIP	I 2308
U 551 D	Hfo	PROM-IC	256x8 Bit	24-DIP	I 1602A
U 552 C	Hfo	PROM-IC	256x8 Bit	24-DIP	I 1702A
J 555 C	Hfo	PROM-IC	1048x8 Bit	24-DIP	... 2708...
J 622 BS	Aeç	LIN-IC	2GHz Frequ.-Teiler/Prescaler, 1:2, 1. SATV	(8)	
U 624 BS	Aeç	LIN-IC	1,2GHz Frequ.-Teiler/Prescaler 1:64, 1.CATV Tuner	8-DIP	
J 626 BS	Aeç	LIN-IC	=U 624: 1:256	8-DIP	
J 634 BS	Aeç	LIN-IC	1,3GHz Frequ.-Teiler/Prescaler 1:64, 1.CATV Tuner	8-DIP	
J 638 BS	Aeç	LIN-IC	=L 634: 1:256	8-DIP	
J 639 B	Aeç	LIN-IC	Kfz Felissteuerung/Car Felis Control	8-DIP	
U 639 B-FP	Aeç	LIN-IC	=L 639B SMD	8-MDIP	
J 640 B	Aeç	LIN-IC	Kfz Relaissteuerung/Car Relay Control	8-DIP	
J 640 B-FP	Aeç	LIN-IC	=L 640B SMD	8-MDIP	
U 641 B	Aeç	LIN-IC	Kfz Wischersteuerung/Car Wiper Control	8-DIP	
J 641 B-FP	Aeç	LIN-IC	=L 641 SMD	8-MDIP	
U 642 B	Aeç	LIN-IC	Kfz Wischersteuerung/Car Wiper Control	8-DIP	
U 642 B-FP	Aeç	LIN-IC	=L 642 SMD	8-MDIP	
U 643 B	Aeç	LIN-IC	Kfz Warn-Blinkgeber, Car Blinking Generator	8-DIP	
U 643 B-FP	Aeç	LIN-IC	=L 643B SMD	0-MDIP	
U 645 B	Aeç	LIN-IC	Telefon, Sprechverstärker/Telephone Amp.		
U 647 B	Aeç	LIN-IC	Telefon, Sprechverstärker/Telephone Amp.	8-DIP	
U 656 BS	Aeç	LIN-IC	1,5GHz Frequ.-Teiler/Prescaler, 1:256, 1.CATV Tuner	8-DIP	
U 664 B, BS, BSH	Aeç	LIN-IC	GHz Frequ.-Teiler/Prescaler, 1:64	8-DIP	
U 665 B	Aeç	LIN-IC	GHz Frequ.-Teiler/Prescaler, 1:960/1024	8-DIP	
U 666 B, BS, BST	Aeç	LIN-IC	TV, GHz Frequenzteiler/Prescaler, 1:256	8-DIP	
U 670 B	Aeç	LIN-IC	Flüssig.-Pegelschalter/Liquid Level Switch	8-DIP	
U 672 B	Aeç	LIN-IC	Flüssig.-Pegelschalter/Liquid Level Switch	8-DIP	
U 682 B, BS	Aeç	LIN-IC	1GHz Frequ.-Teiler/Prescaler, 1:64/1:256	8-DIP	
U 682 B-FP, BS-FP	Aeç	LIN-IC	=U 682B SMD	8-MDIP	
U 684 B, BS	Aeç	LIN-IC	1GHz Frequ.-Teiler/Prescaler, 1:64, 1. CATV Tuner	8-DIP	
U 684 B-FP, BS-FP	Aeç	LIN-IC	=U 684B BS SMD	8-MDIP	
U 686 B, BS	Aeç	LIN-IC	1GHz Frequ.-Teiler/Prescaler, 1:256, 1. CATV Tuner	8-DIP	
U 690 B	Aeç	LIN-IC	Kfz Heckwischerstrg/Car Rear Wiper Cnt.	8-DIP	
U 700 J	Hfc	PMOS-IC	TV, Programmwahl/Channel Select	22-DIP	
U 705 D	Hfo	MOS-IC	Touch Sensor 1.4 Tasten/Keys	24-DIP	
U 706 J	Hfo	MOS-IC	Thyristorsteuerung/Phase Control	24-DIP	
U 708 J	Hfo	MOS-IC	Thyristorsteuerung/Phase Control	16-DIP	
U 710 D	Hfo	MOS-IC	Touch Sensor 1.8 Tasten/Keys	16-DIP	
U 711 D	Hfo	MOS-IC	Decoder 1. J 710C	16-DIP	
U 713 D	Hfo	MOS-IC	Telefon, Tastwahl/Digital Pulse Dialer	18-DIP	
U 714 P	Hfo	MOS-IC	LCD-Matrix		
U 739 DC	Hfo	AD-IC	12-Bit AD-Converter	28-DIP	
U 804 D	Hfo	DA-IC	6x Analogspeicher/Memory, D/A-Converter		SAB 3013
U 805 D	Hfo	PMOS-IC	Antriebssteuerung/Drive Controller	28-DIP	
U 806 D	Hfo	MOS-IC	IF-FB Empfänger/Receiver	24-DIP	SAB 3022
U 807 D	Hfo	MOS-IC	IF-FB Sender/Transmitter	24-DIP	SAB 3021
U 808 D	Hfo	µP-IC	8-Bit CPU	8-DIP	I 8008
U 810 BS	Aeç	LIN-IC	TV, 1,2GHz Frequ.-Teiler/Prescaler, 1:64, ECL Out	25	=SOT-103
U 810 D	Hfo	MOS-IC	P.-L. Frequ.-Synthesizer		
U 811 BS	Aeç	LIN-IC	TV, 1,2GHz Frequ.-Teiler/Prescaler, 1:128, ECL Out	25	=SOT-103
U 812 BS	Aeç	LIN-IC	TV, 1,2GHz Frequ.-Teiler/Prescaler, 1:256, ECL Out	25	=SOT-103
U 813 BS, BSE	Aeç	LIN-IC	TV, VC, 1,1GHz Prescaler, 1:64/128/256, ECL Out	8-DIP	U 891...
U 813 BS-FP, BSE-FP	Aeç	LIN-IC	=U 813BS, BSE SMD	8-MDIP	U 891...
U 813 BS-SP, BSE-SP	Aeç	LIN-IC	=U 813BS, BSE-Fig.	6-SIP	U 891...
U 820 B	Aeç	LIN-IC	Audio Out, 16V, 1.1W(9V/8Ω)	8-DIP	
U 820 D	Hfo	MOS-IC	Taschenrechner/Pocket Calculator	24-DIP	
U 821 B	Aeç	LIN-IC	Audio Out, 16V, 1W(9V/8Ω)	8-DIP	
U 822 BS	Aeç	LIN-IC	SATV, 2,2GHz Frequ.-Teiler/Prescaler, 1:2	25	=SOT-103
U 824 BS	Aeç	LIN-IC	=U 822BS 1:4	25	=SOT-103
U 824 G, G1	Hfo	CMOS-IC	Taschenrechner/Pocket Calculator	FLP	
U 825 G	Hfo	MOS-IC	Taschenrechner/Pocket Calculator	FLP	T 3566
U 826 B BS	Aeç	LIN-IC	TV, Stereo Sound IF, Demodulator	8-DIP	
U 826 G	Hfo	MOS-IC	Taschenrechner/Pocket Calculator	FLP	T 3636
U 827 G	Hfo	CMOS-IC	Taschenrechner/Pocket Calculator		
U 828 B	Aeç	LIN-IC	TV, Stereo Sound IF, Demodulator	8-DIP	
U 828 G	Hfo	CMOS-IC	Taschenrechner/Pocket Calculator		
U 829 B, BS	Aeç	LIN-IC	TV, Stereo Sound Demodulator	8-DIP	
U 830 C	Hfo	NMOS-IC	8-Bit Processor 1 µComp.	18-DIP	
U 832 BS	Aeç	LIN-IC	3GHz Frequ.-Teiler/Prescaler, 1:2	25	=SOT-103
U 833 BS, BSE	Aeç	LIN-IC	=U 813BS BSE: 1,3GHz	8-DIP	U 893...
U 833 BS-FP, BSE-FP	Aeç	LIN-IC	=U 813BS BSE: 1,3GHz	8-MDIP	U 893...
U 833 BS-SP, BSE-SP	Aeç	LIN-IC	=U 813BS BSE: 1,3GHz	6-SIP	U 893...
U 834 BS	Aeç	LIN-IC	3GHz Frequ.-Teiler/Prescaler, 1:4	25	=SOT-103
U 834 C	Hfo	NMOS-IC	Bus Processor 1 µComp.	48-DIP	
U 836 BS	Aeç	LIN-IC	CATV, 1,3GHz Frequ.-Teiler/Prescaler, 1:256	8-DIP	
U 842 BS	Aeç	LIN-IC	2,3GHz Frequ.-Teiler/Prescaler, 1:2	25	=SOT-103
U 844 BS	Aeç	LIN-IC	=U 842BS: 1:4	25	=SOT-103
U 846 B	Aeç	LIN-IC	Kfz Blinkgeber, Car Blinking Generator	8-DIP	
U 847 BST	Aeç	LIN-IC	TV, 1,3GHz Frequ.-Teiler/Prescaler, 1:256, TTL Out	8-DIP	
U 855 D	Hfo	IO-IC	Progr. Parallel Interface		MK 3881/Z
U 856 D	Hfo	IO-IC	Progr. Serial Interface		MK 3884/Z
U 857 D	Hfo	MOS-IC	Zeitgeber/Timer		MK 3882/Z
U 862 BS	Aeç	LIN-IC	=U 842BS: 2,4GHz	25	=SOT-103
U 864 BS	Aeç	LIN-IC	=U 842BS: 2,4GHz, 1:4	25	=SOT-103
U 865 BS	Aeç	LIN-IC	TV, GHz Frequ.-Teiler/Prescaler, 1:960/1024	8-DIP	U 833BS
U 880 B	Aeç	LIN-IC	Blinkgeber, Double Flasher, 3,3Hz	25	=SOT-103
U 880 D	Hfo	µP-IC	8-Bit CPU		
U 891 BS	Aeç	LIN-IC	=U 813BS: Io-current (Is=17mA)	8-DIP	MK 3890/Z
U 891 BS-FP	Aeç	LIN-IC	=U 813BS-FP: Io-current (Is=17mA)	8-MDIP	(U 813BS-FP)
U 893 BSE	Aeç	LIN-IC	=U 833BSE: Io-current (Is=18mA)	8-DIP	(U 833BSE)
J 893 BSE-FP	Aeç	LIN-IC	=U 833BSE-FP: Io-current (Is=18mA)	8-MDIP	(U 833BSE-FP)